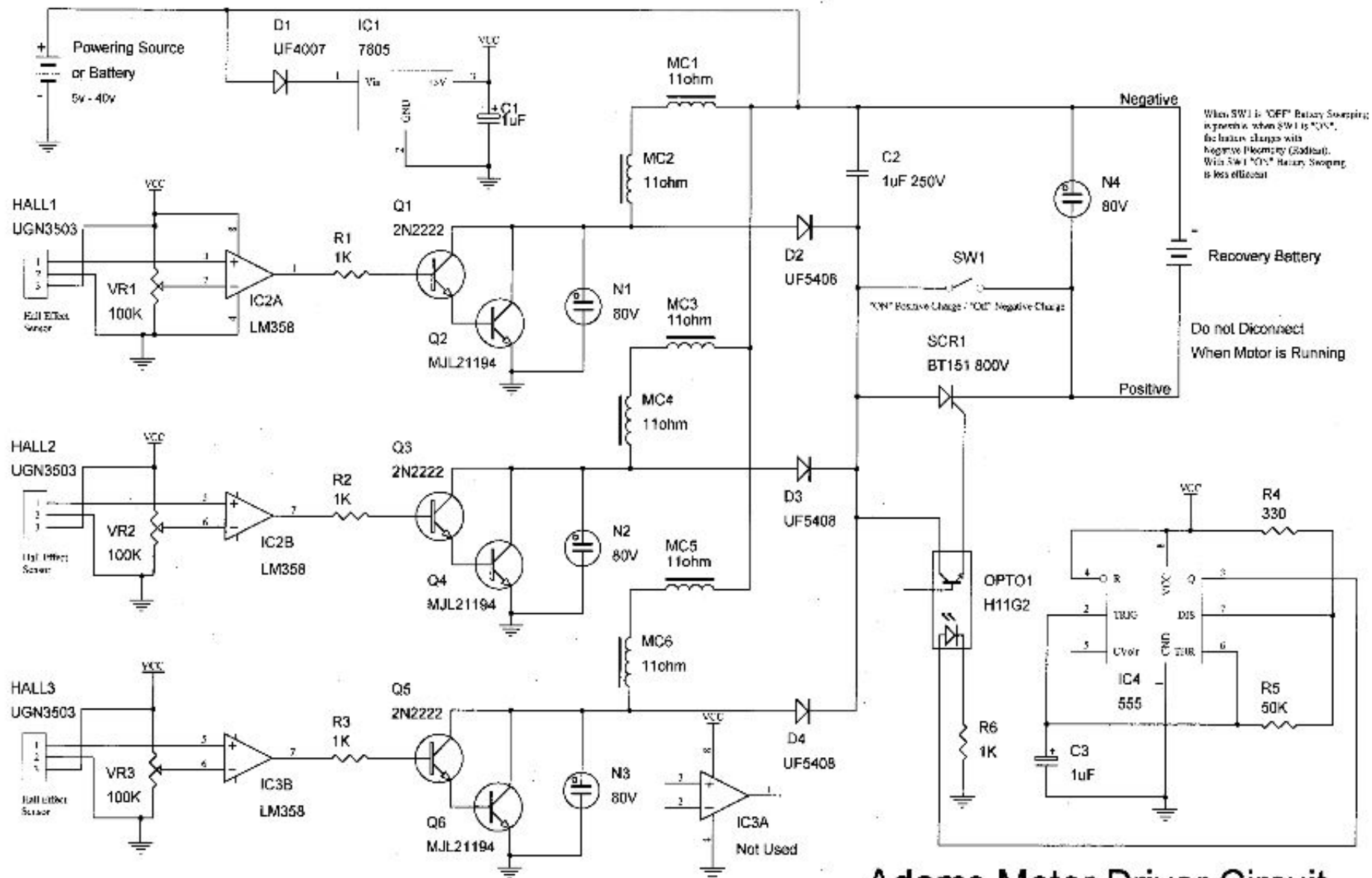




Adams Motor Driver Circuit

by N_tech0